

Roll No. ....

**Y- 3632 (A)**

**B.C.A. (Second Semester) (SPECIAL) EXAMINATION, August 2021**

**[SECOND CHANCE]**

**PAPER—202**

**Computer Organization**

*Time : Three Hours*

*Maximum Marks : 80*

*Minimum Pass Marks : 32*

**Note**—Attempt *all* questions.

1. (a) State and explain Duality theorem. Give suitable example. 8  
(b) Write explanatory short notes on any *two*— 8
  - (i) Universal gates and their use.
  - (ii) Difference between ordinary algebra and Boolean algebra.
  - (iii) Demorgan's theorem and its use.
2. (a) Giving neat diagram, explain the working principle and use of Decoder. 8  
(b) Use a Karnaugh map to minimise the following standard POS expression : 8
$$(A+B+C) \times (A+B+\bar{C}) \times (A+\bar{B}+C) \times (A+\bar{B}+\bar{C}) \times (\bar{A}+\bar{B}+C)$$
3. Giving neat diagram and uses, write short notes on the following : 16
  - (i) Encoder
  - (ii) Multiplexer
  - (iii) K-map
4. Giving neat diagram and suitable examples, write short notes *on any four* of the following : 16
  - (i) Advantages of 2's complement usage over 1's complement.
  - (ii) Sign magnitude numbers.
  - (iii) Half Adder and its use

**P.T.O.**

- (iv) Full Adder and its use.
  - (v) Circuits for Binary Arithmetic.
  - (vi) Over flow—its cause and applications.
5. (a) Giving neat circuit diagram, explain the working principle and use of master-slave flip-flop. 8
- (b) Giving symbol, truth table and uses, explain the working principle of any *two* of the following : 8
- (i) R-S flip-flop.
  - (ii) Shift registers
  - (iii) J-K flip-flop.