

Roll No.

Y – 3632

B.C.A. (Second Semester) EXAMINATION, May/June-2021

Paper – 202

COMPUTER ORGANIZATION

Time : Three Hours

Maximum Marks : 80

Minimum Pass Marks : 32

Note—Attempt *all* questions.

Unit-I

1. (a) State and prove Demorgan's theorem. Using Demorgan's theorem, show that— 8
 - (a) $A + AB = A$
 - (b) $(A + B)(A + C) = A + BC$
- (b) Draw all logic gates. Give their truth table and symbols. Mention their uses. 8

Unit-II

2. Giving neat diagram and uses, write short notes on any **four** of the following— 16
 - (a) Encoder.
 - (b) Demultiplexer.
 - (c) Multiplexer
 - (d) K-map
 - (e) Seven segment decoder
 - (f) Grey code and its use.

Unit-III

3. (a) Giving symbol and truth table, explain the working of a full adder. List its uses. Discuss how it differs from Half adder. 8
- (b) Giving suitable examples, explain the following— 8
 - (a) Subtractor circuits.
 - (b) Over flow.List their practical uses.

P.T.O.

Unit-IV

4. Giving neat diagram and examples, write short notes on any **four** of the following— 16
- (a) Asynchronous counter.
 - (b) Synchronous counter.
 - (c) Clock edge triggered flip-flop.
 - (d) Buffer Registers.
 - (e) Ring counter.
 - (f) R-S flip-flop.

Unit-V

5. Write explanatory short notes, with suitable example and/or diagram, on any **four** of the following— 16
- (a) Comparison between magnetic core and semiconductor memory.
 - (b) DRAMS and SRAMS.
 - (c) D to A and A to D Converter.
 - (d) Magnetic disk.
 - (e) Memory cells.
 - (f) Memory Addressing.
 - (g) PROMS and EPROMS.